



2023 ICS 期中考试

B2, B3, B4

汤皓宇


2023 年 12 月 1 日

- B2, B3, B4 部分主要考察组合与时序电路、状态机的知识。
- 对组合电路中一些运算的规律掌握不是很熟练，比如摩根律、结合律、排中律、双重否定律等。
- 画逻辑电路图时出现遗漏符号的问题。
- 对时序电路的分析不太熟练。
- 状态机的绘制容易出现遗漏、不标状态转移条件等问题。

B2

B2 (1)

 Please write the logic expression for the circuit below.



答案

简记 $X Y$, $X + Y$, \bar{X} 分别表示 X AND Y , X OR Y , NOT X .

$$\begin{aligned} L &= \bar{A} \bar{B} \bar{C} + A \bar{B} \bar{C} + \bar{A} \bar{B} D \\ &= \bar{B} \bar{C} + \bar{A} \bar{B} D \\ &= \bar{B}(\bar{C} + \bar{A} D) \end{aligned}$$

B2 (2) 出题人思路

$$\begin{aligned}L &= \bar{A} \bar{B} \bar{C} + A \bar{B} \bar{C} + \bar{A} \bar{B} D \\&= \bar{B} \bar{C} + \bar{A} \bar{B} D \\&= \bar{B}(\bar{C} + \bar{A} D)\end{aligned}$$

Rewrite the expression using only NOT and NAND.

答案

三输入与非门可以使用记号 $NAND(X, Y, Z)$ 或者直接 \overline{XYZ} , 注意 NAND 没有结合律。

$$\begin{aligned}L &= \bar{A} \bar{B} \bar{C} + A \bar{B} \bar{C} + \bar{A} \bar{B} D \\&= \overline{\overline{\bar{A} \bar{B} \bar{C}} + \overline{A \bar{B} \bar{C}} + \overline{\bar{A} \bar{B} D}} \\&= \overline{\bar{A} \bar{B} \bar{C} A \bar{B} \bar{C} \bar{A} \bar{B} D}\end{aligned}$$

B2 (2) 非预期解

$$\begin{aligned}L &= \bar{A} \bar{B} \bar{C} + A \bar{B} \bar{C} + \bar{A} \bar{B} D \\&= \bar{B} \bar{C} + \bar{A} \bar{B} D \\&= \bar{B}(\bar{C} + \bar{A} D)\end{aligned}$$

Rewrite the expression using only NOT and NAND.

答案 1

$$\begin{aligned}L &= \bar{B} \bar{C} + \bar{A} \bar{B} D \\&= \overline{\overline{\bar{B} \bar{C} + \bar{A} \bar{B} D}} \\&= \overline{\bar{B} \bar{C} \bar{A} \bar{B} D}\end{aligned}$$

答案 2

$$\begin{aligned}L &= \bar{B}(\bar{C} + \bar{A} D) \\&= \overline{\overline{\bar{B}(\bar{C} + \bar{A} D)}} \\&= \overline{\bar{B} \bar{C} \bar{A} D}\end{aligned}$$

B2 (2) 只使用二输入门

答案

$$\begin{aligned} L &= \overline{A} \overline{B} \overline{C} + A \overline{B} \overline{C} + \overline{A} \overline{B} D \\ &= \overline{\overline{\overline{A} \overline{B} \overline{C}}} + \overline{\overline{\overline{A} \overline{B} \overline{C}}} + \overline{\overline{\overline{A} \overline{B} D}} \\ &= \overline{\overline{\overline{\overline{A} \overline{B} \overline{C}} \overline{\overline{\overline{A} \overline{B} \overline{C}}}}} + \overline{\overline{\overline{A} \overline{B} D}} \\ &= \overline{\overline{\overline{\overline{\overline{A} \overline{B} \overline{C}} \overline{\overline{\overline{A} \overline{B} \overline{C}}}}} + \overline{\overline{\overline{A} \overline{B} D}} \\ &= \overline{\overline{\overline{\overline{\overline{A} \overline{B} \overline{C}} \overline{\overline{\overline{A} \overline{B} \overline{C}} \overline{\overline{\overline{A} \overline{B} D}}}}} \\ &= \text{NAND}(\text{NOT}(\text{NAND}(\text{NAND}(\text{NOT}(\text{NAND}(\text{NOT}(A), \text{NOT}(B))), \text{NOT}(C)), \\ &\quad \text{NAND}(A, \text{NOT}(\text{NAND}(\text{NOT}(B), \text{NOT}(C))))) \\ &\quad \text{NAND}(\text{NOT}(\text{NAND}(\text{NOT}(A), \text{NOT}(B))), D)) \end{aligned}$$


B2 (3)

$$L = \overline{\overline{\overline{A} \overline{B} \overline{C}} \overline{A} \overline{B} \overline{C} \overline{A} \overline{B} \overline{D}}$$

Draw the logic diagram implemented using only NOT gates and NAND gates.

答案

其他的表达式对应的逻辑电路图也对，这里只给出一种。

 

B3

Use only **NOT** gates and **2-input NOR** gates to draw a logic circuit diagram for expression $L = A \bar{B} + \bar{A} C$.


答案

$$\begin{aligned} L &= A \bar{B} + \bar{A} C \\ &= \overline{\overline{A \bar{B}} + \overline{\bar{A} C}} \\ &= \overline{\overline{A} + B + \overline{A} + C} \end{aligned}$$

$$L = \overline{\overline{\overline{A} + B + A + C}}$$

Use only **NOT** gates and **2-input NOR** gates to draw a logic circuit diagram for expression $L = A \overline{B} + \overline{A} C$.

答案

 

B4

Please explain why state machines must be implemented using sequential circuits and cannot be realized with only combinational circuits.


答案

状态机的输出不止和当前的输入有关，也与之前的输入有关，因此需要使用时序电路来存储之前的状态；而组合电路不能保存之前的状态，输出只和输入有关。

B4(2)

D-trigger, is a type of digital storage element in digital circuits. It has three inputs: a data input (D), clear input (R) and a clock input (CLK). When the clear signal (R) is asserted, it forces the output (Q) to be '0'. The clock input determines when the data input should be sampled. When clock signal rising edge occurs, it will make $Q = D$.

 Your job: Describe what the following sequential circuit does in **one sentence**. Assume that the output $Q_0Q_1Q_2Q_3$ is initially 0000.



答案

在时钟 CP 下降沿到来时, 输出 $Q_3Q_2Q_1Q_0$ 会增加 1, 且可以循环。


B4(3)

Design a Finite State Machine (FSM) that recognizes patterns of "000" and "010" in an input string and outputs 1 when either pattern is detected.

For example, given a string 00001000, it will produce 00110101.

答案

每个状态都需要考虑所有的可能输入，即每个状态会有两条出边。

 


B4(3) 另一种

Design a Finite State Machine (FSM) that recognizes patterns of "000" and "010" in an input string and outputs 1 when either pattern is detected.

For example, given a string 00001000, it will produce 00110101.

答案

 

Questions?

谢谢大家
